

**Welcome to my
Presentation**

Presentation on Digital Logic Design

Presented By:

Name : Tushar Sarkar

Student ID: 18CSE035

Second Year First Semester

Department of CSE,BSMRSTU,

Gopalganj-8100.

Outline

- ❖ Question
- ❖ Converting Excess-3 to BCD(8421)
- ❖ Converting Table Excess-3 to BCD(8421)
- ❖ K-Map for A
- ❖ K-Map for B
- ❖ K-Map for C
- ❖ K-Map for D
- ❖ Minimized Boolean expressions
- ❖ Logic Diagram

My Question is 4

Design of a combinational circuit that converts excess-3 code to BCD with a 4-bit adder and external gates.

Converting Excess-3 to BCD(8421)

- ❖ Excess-3 code can be converted back to BCD in the same manner.
- ❖ Let A, B, C & D be the bits representing the binary numbers, where D is the LSB and A is the MSB.
- ❖ Let w, x, y & z be the bits representing the gray code of the binary numbers, where z is the LSB and w is the MSB.
- ❖ The truth table for the conversion is given below.
- ❖ The X's mark don't care conditions.

Converting Table Excess-3 to BCD(8421)

Excess-3				BCD			
w	x	y	z	A	B	C	D
0	0	0	0	X	X	X	X
0	0	0	1	X	X	X	X
0	0	1	0	X	X	X	X
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

K-Map for A


<div>WX \ YZ</div>	00	01	11	10
00	X	X	0	X
01	0	0	0	0
11	1	X	X	X
10	0	0	1	0

WX


WYZ

$$A = WX + WYZ$$

K-Map for B

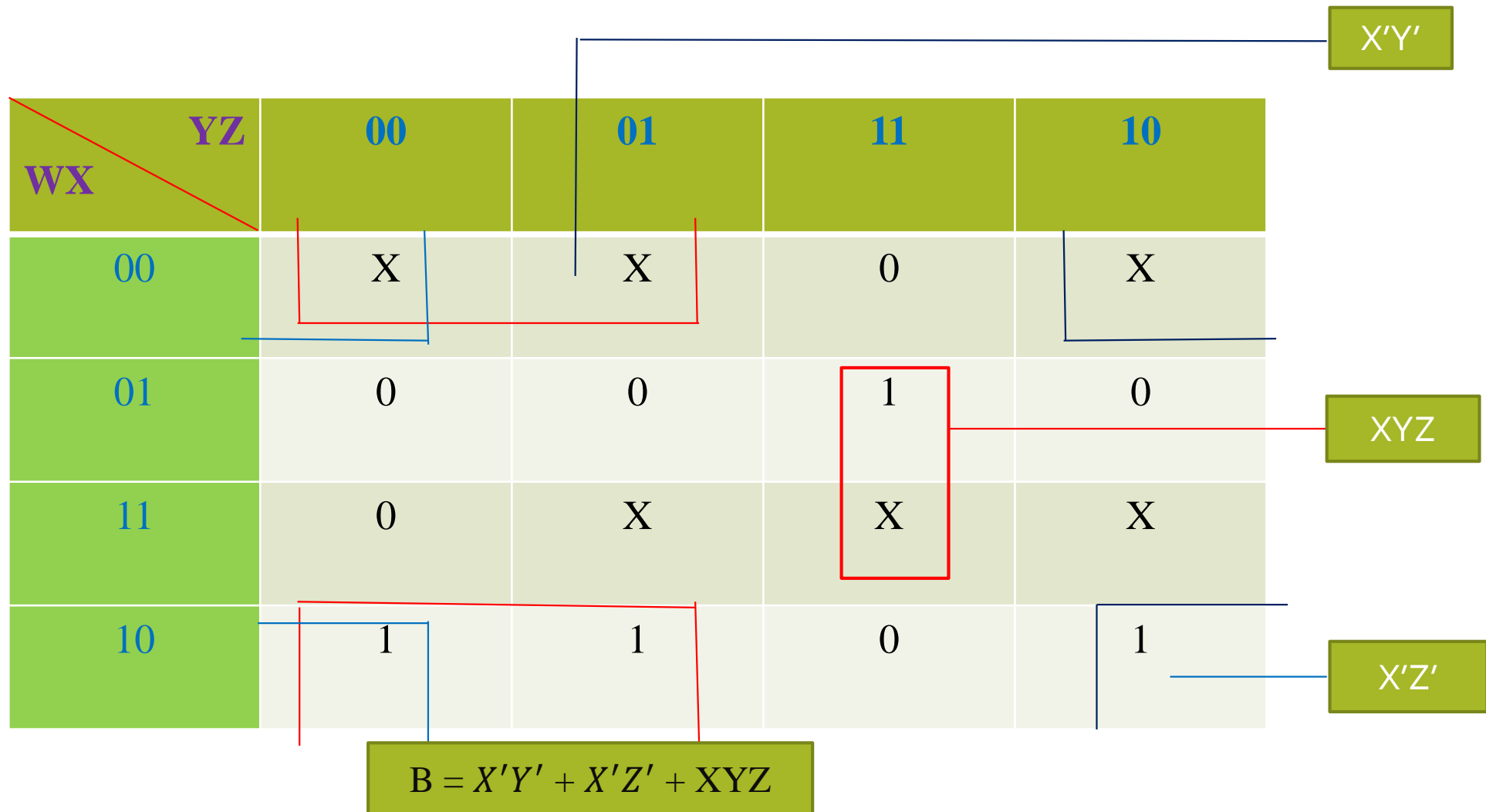

K-Map for C

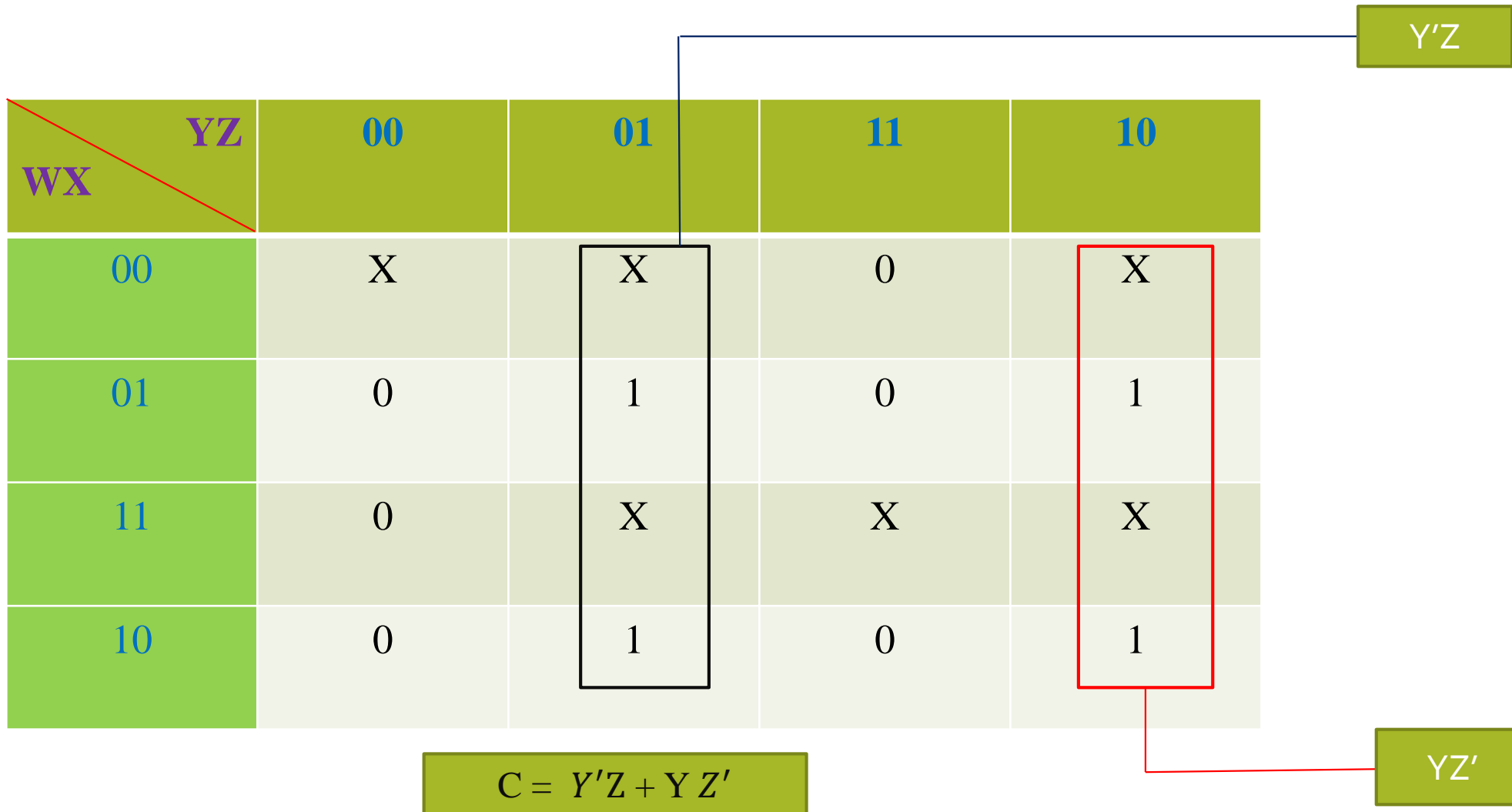

K-Map for D

$WX \backslash YZ$	00	01	11	10
00	X	X	0	X
01	1	0	0	1
11	1	X	X	X
10	1	0	0	1

Z'

$D = Z'$

Minimized Boolean express

- ✓Corresponding minimized Boolean expressions for Excess-3 code bits

$$A = WX + WYZ$$


$$B = X'Y' + X'Z' + XYZ$$

$$C = Y'Z + YZ'$$

$$D = Z'$$

Logic Diagram
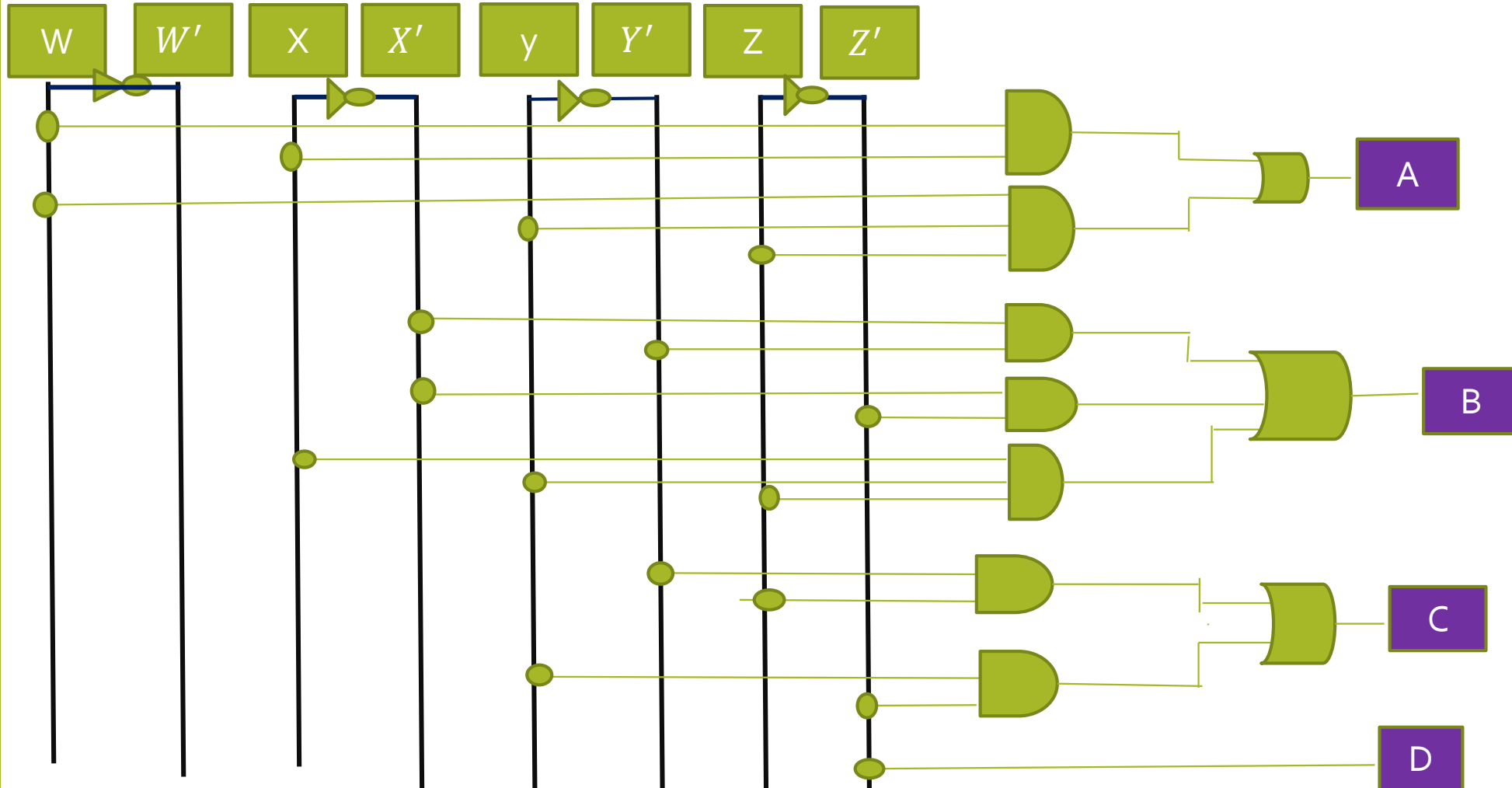
$$A = WX + WYZ, \quad B = X'Y' + X'Z' + XYZ, \quad C = Y'Z + YZ', \quad D = Z'$$



Thank You