

**Welcome to my
Presentation**

Presentation on Digital Logic Design

Presented By:

Name : Tushar Sarkar

Student ID: 18CSE035

Second Year First Semester

Department of CSE,BSMRSTU,

Gopalganj-8100.

Outline

- ❖ Question
- ❖ F_1 And F_2 Determine
- ❖ F'_1 And F'_2 Determine
- ❖ PLA Program Table
- ❖ Logic Diagram

My Question is 5

Implementation of a circuit with a PLA having three inputs, four products terms and two outputs for the following functions:

$$F_1 = \sum(0,1,2,4)$$

$$F_2 = \sum(0,5,6,7)$$

F_1 and F_2 Determination

$\begin{array}{c} \text{BC} \\ \diagdown \\ \text{A} \end{array}$	00	01	11	10
0	1	1		1
1	1			

$$F_1 = A'B' + A'C' + B'C'$$

$\begin{array}{c} \text{BC} \\ \diagdown \\ \text{A} \end{array}$	00	01	11	10
0	1			
1		1	1	1

$$F_2 = A'B'C' + AC + BC$$

F'_1 and F'_2 Determination

$\begin{array}{c} \text{BC} \\ \text{A} \end{array}$	00	01	11	10
0			0	
1		0	0	0

$$F'_1 = (AB + AC + BC)$$

$$F_1 = (AB + AC + BC)'$$

$\begin{array}{c} \text{BC} \\ \text{A} \end{array}$	00	01	11	10
0		0	0	0
1	0			


$$F'_2 = (AB'C' + A'C + A'B)$$

$$F_2 = (AB'C' + A'C + A'B)'$$

PLA Program Table

Product Terms	INPUT			OUTPUT		
	A	B	C	F_1	F_2	
AB	1	1	-	1	1	
AC	1	-	1	1	1	
BC	-	1	1	1	-	
$A'B'C'$	0	0	0	0	1	
				C	T	T/C

Logic Diagram

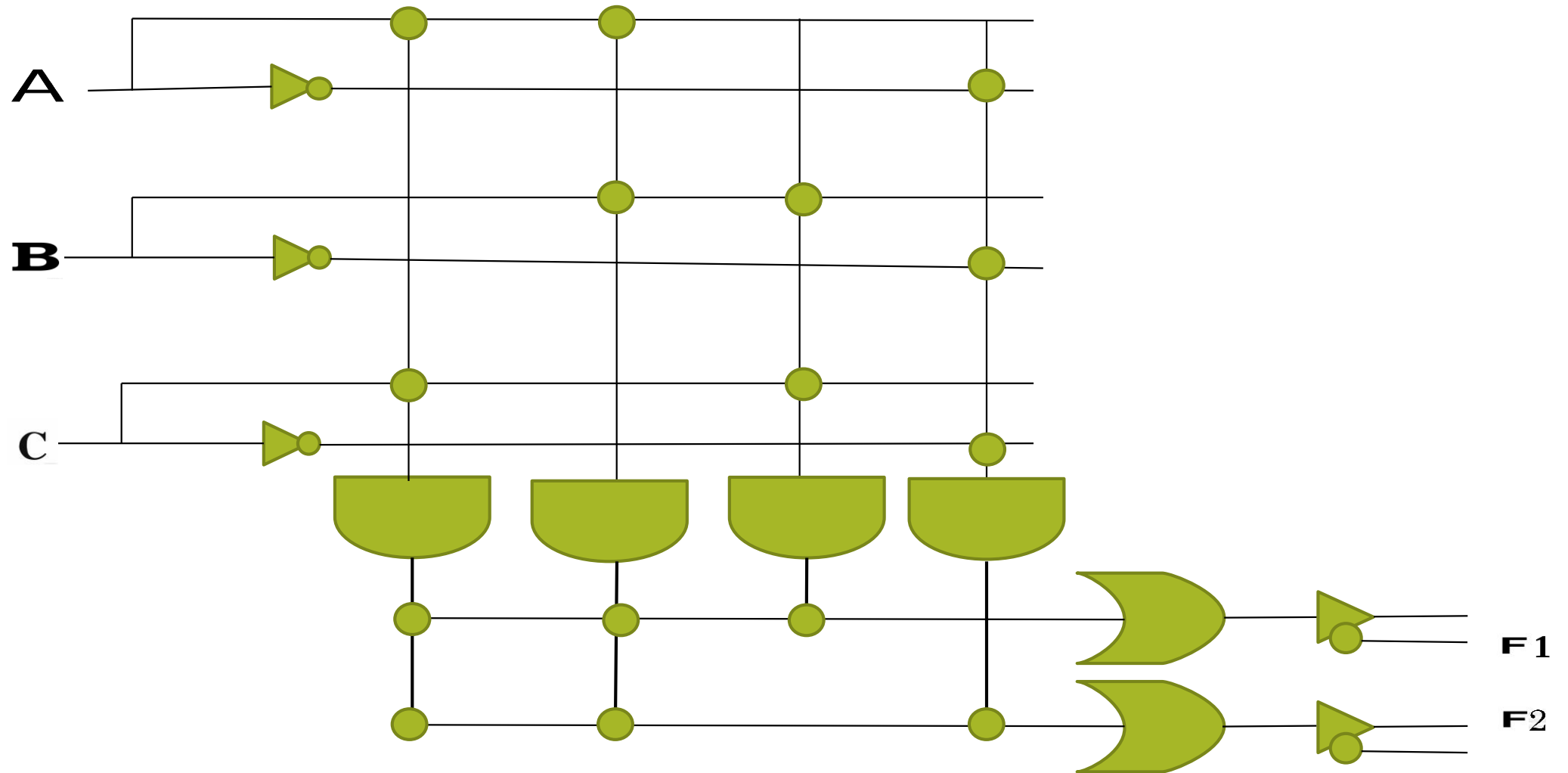

Thank You