



Welcome To My Presentation

My Presentation Topics is

Flip Flops & The Practical use Cases

Presented By

Tushar Sarkar

Student ID : 18CSE035

Second Year Second Semester

Department of CSE, BSMRSTU.

Content

- ❑ What is Flip flop?
- ❑ Types Of Flip Flop
- ❑ SR Flip Flop
- ❑ D Flip Flop
- ❑ JK Flip Flop
- ❑ T Flip Flop
- ❑ The Practical Uses of Flip Flop

What is Flip Flop?

- ▶ A flip flop is an electronic circuit with two stable states that can be used to store binary data, bit 1 or bit 0.
- ▶ The stored data can be changed by applying varying inputs.
- ▶ The designing of the flip flop circuit can be done by using logic gates such as two NAND and NOR gates.
- ▶ Each flip flop consists of two inputs and two outputs, namely set and reset, Q and Q'.
- ▶ This kind of flip flop is stated to as an SR flip flop.


Types of Flip Flop

- ▶ Flip flop circuits are classified into four types based on its use, Namley-

- SR-Flip Flop
- D Flip Flop
- JK Flip Flop
- T Flip Flop


SR Flip Flop

- ▶ The SR-flip flop is built with two AND gates and a basic NOR flip flop.
- ▶ The o/ps of the two AND gates remain at 0 as long as the CLK pulse is 0, irrespective of the S and R i/p values.
- ▶ When the CLK pulse is 1, information from the S and R inputs permits through the basic FF.
- ▶ When $S=R=1$, the clock pulse occurrence roots both the o/ps go to 0.
- ▶ When the CLK pulse is detached, the state of the FF is unstated.

 


SR Flip Flop

NAND Gate SR Flip-flop :

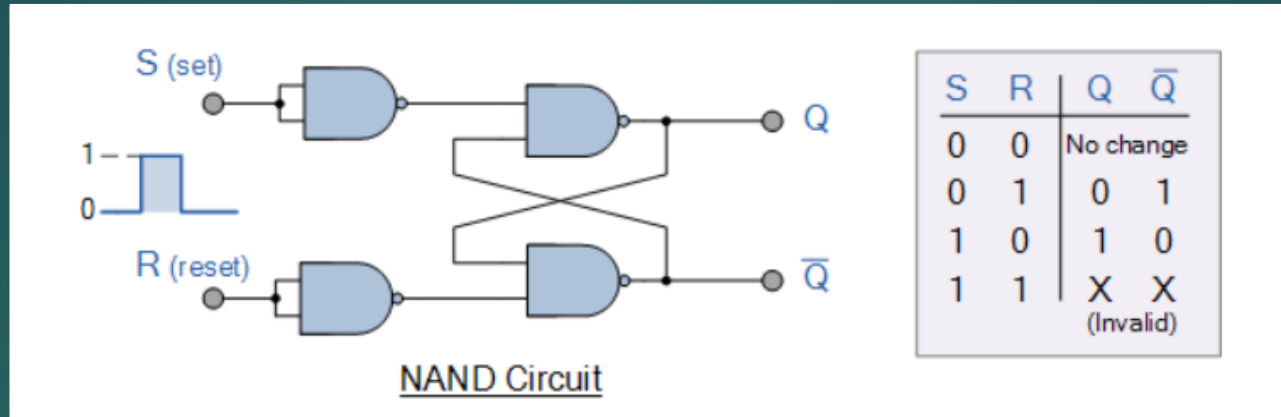


NOR Gate SR Flip-flop

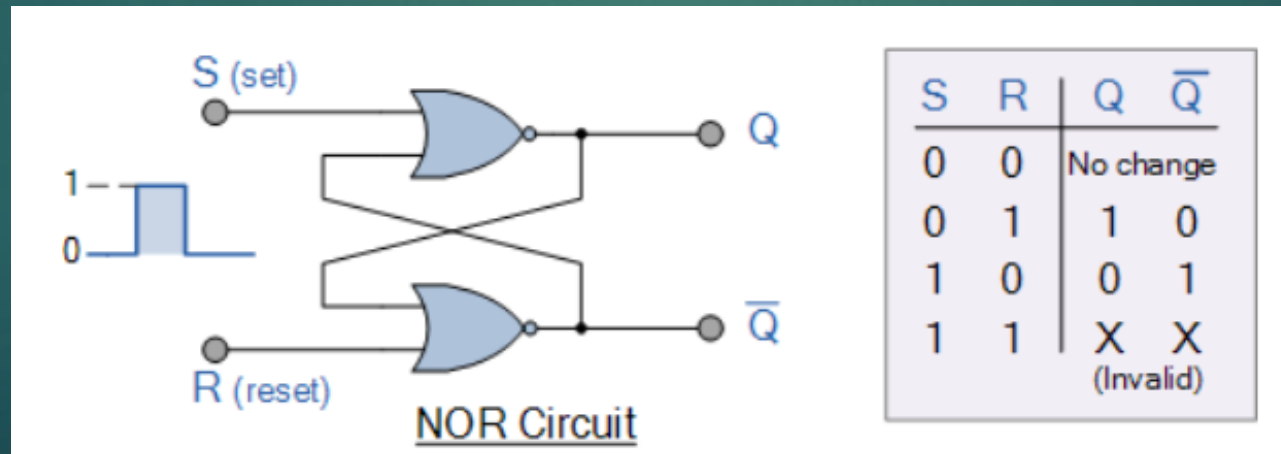

JK Flip Flop


- ▶ A JK-FF is a simplification of the SR-flip flop. The inputs of the J and K flip flops behave like the inputs S & R.
- ▶ When input 1 is applied to both the inputs J and K, then the FF switches to its complement state. The designing of the JK FF can be done in such a way that the o/p Q is ANDed with P and.
- ▶ This procedure is made so that the FF is cleared during a CLK pulse only if the output was previously 1. In the same way, the output is ANDed with J & CP so that the FF is cleared during a CLK pulse only if Q' was previously 1.

 

Symbol

JK Flip Flop

JK flip Flop Logic Diagram:

 


Truth Table for JK Flip Flop :


Input			Output		
Clk	J	K	Q	Q'	Status
↑	0	0	Q	Q'	No Change
↑	0	1	1	0	Reset
↑	1	0	0	1	Set
↑	1	1	Q'	Q	Toggle

D Flip Flop

 - ▶ D Flip Flop also known as Data Flip Flop
- ▶ The D-input is sampled throughout the existence of a CLK pulse.
- ▶ If it is 1, then the FF is switched to the set state.
- ▶ If it is 0, then the FF switches to a clear state.
- ▶ The D flip flop will act as a storage element for a single binary digit (Bit)




D Flip Flop

 

Input		Output	
Clk	D	Q	Q'
↓ >> 0	0	0	1
↑ >> 1	0	0	1
↓ >> 0	1	0	1
↑ >> 1	1	1	0


T Flip Flop

- ▶ The T-flip flop or toggle flip flop is a single i/p version of the JK-flip flop.
- ▶ The working of this FF is as follows: When the input of the T is '0' such that the 'T' will make the next state that is similar to the current state.
- ▶ That means when the input of the T-FF is 0 then the present state and the next state will be 0.
- ▶ However, if the i/p of the T is 1 then the present state is inverse to the next state. That means, when $T=1$, then the present state = 0 and next state = 1).

 

T Flip Flop

T flip Flop Logic Diagram:

 

Truth Table for T Flip Flop :

Input		Output		
T	Clk	Q	Q'	Status
0	↑	Q	Q'	Hold
1	↑	Q'	Q	Togol

The Practical Uses of Flip Flop

▶ Counters-

Asynchronous counter

Modulo – n – counter

Synchronous counter

2 – Bit synchronous counter

Applications of Counters

▶ Registers.

▶ Frequency Division.

▶ Data Transfer.



Thank You