

**Welcome to my  
Presentation**

# Presentation on Digital Logic Design

## **Presented By:**

Name : Tushar Sarkar

Student ID: 18CSE035

Second Year First Semester

Department of CSE,BSMRSTU,

Gopalganj-8100.

# My Question is 2

- Design of a combinational circuit with a decoder and external gates for the following three Boolean functions:

$$F_1 = X'Y'Z' + YZ$$

$$F_2 = X'YZ' + X'Z$$

$$F_3 = XYZ' + Z$$

$$F_1 = X'Y'Z' + YZ$$

$$= X'Y'Z' + YZ(X+X')$$

$$= X'Y'Z' + XYZ + X'YZ$$

$$= \Sigma(0,3,7)$$

$$F_2 = X'YZ' + X'Z$$

$$= X'YZ' + X'Z(Y + Y')$$

$$= X'YZ' + X'YZ + X'Y'Z$$

$$= \Sigma(1, 2, 3)$$


$$F_3 = XYZ' + Z$$

$$= XYZ' + Z(X+X')(Y+Y')$$

$$= XYZ' + XYZ + XY'Z + X'YZ + X'Y'Z$$

$$= \sum(1,3,5,6,7)$$

## Decoder To External

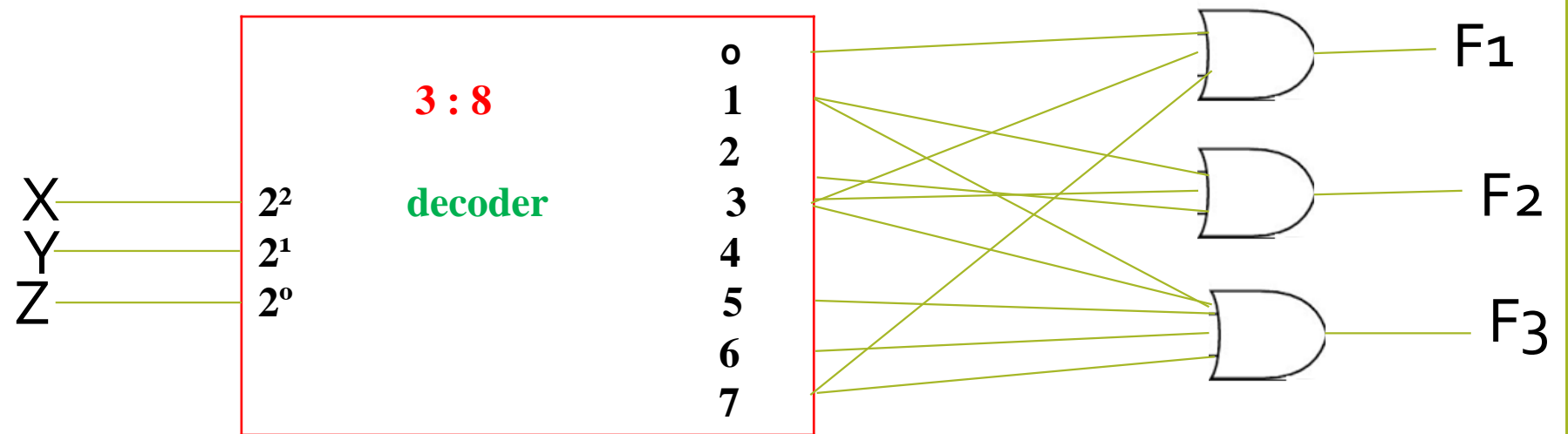

*Thank You*